

16-BIT MICROPROCESSOR USING VERILOG

EC-448 Major Project

By Soham Patel (16EC085)

CONTENTS

- Objective
- Specifications
- Instruction Table
- Blocks developed
- Discussion and test of components
- Test programs
- Limitations
- References

OBJECTIVE

- To design a 16-bit microprocessor (RISC)
- Develop using Xilinx ISE Design Suite and verilog HDL

SPECIFICATIONS

- 16-bit instruction set
- Interface 64k memory
- ALU supports signed binary
- Harvard Architecture
- 8 general purpose registers
- 18 executable instructions

INSTRUCTION TABLE

Sr. No	Instruction Type	Instruction	1st Cycle		2nd Cycle		Information
			1st Byte (reg)	2nd Byte (opcode)	2 Bytes (data/addr)		
1	Load / Store operations	LDM	00 to 07	01	Address		Loads data from memory address to register
2		LDR	00 to 07 (source)	02	00	00 to 07 (other)	Loads data from source register to other register
3		LDV	00 to 07	03	Data		Loads data to register
4		STR	00 to 07	04	Address		Stores data from register to memory address
5	Arithmetic operations	ADR	00	10	0000		Adds data from reg 0 and reg 1
6		ADD	00	11	Data		Adds data to accumulator (reg 0)
7		SBR	00	12	0000		Subtracts data in reg 0 from reg 1 (r0 - r1)
8		SUB	00	13	Data		Subtracts data in accumulator (r0) from given data
9		INC	00	14	0000		Increments the value of accumulator (r0) by 1
10		DEC	00	15	0000		Decrements the value of accumulator (r0) by 1
11	Logical operations	XOR	00	1f	Data		Performs xor operation on accumulator and given data
12		AND	00	1e	Data		Performs and operation on accumulator and given data
13		OR	00	1d	Data		Performs or operation on accumulator and given data
14		XNOR	00	1c	Data		Performs xnor operation on accumulator and given data
15		NAND	00	1b	Data		Performs nand operation on accumulator and given data
16		NOR	00	1a	Data		Performs nor operation on accumulator and given data
17	Other operation	INV	00	19	0000		Performs inverter operation on accumulator
18		NOP	00	00	0000		Performs no operation
19		REG	00 to 07	ff	0000		Loads data of source register on data bus


BLOCKS DEVELOPED

- ALU
- Instruction Register
- Program Counter
- Memory
- Flag Register
- Decoder
- General Purpose Register
- Top module

ALU

- Verilog functions (add, inv, 2's comp)
- I/O 16-bit SM format
- 2's comp
- 2 modes (A and L)
- Around 15 functions
- Carry look-ahead adder

ArithmeticLogicUnit

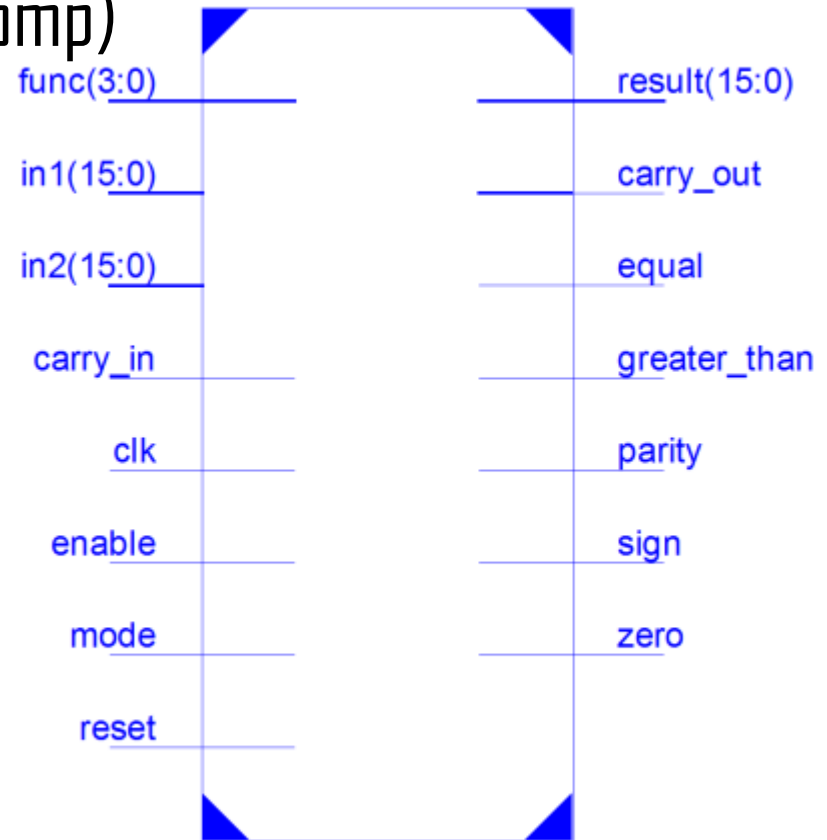


ArithmeticLogicUnit


ALU FUNCTIONS

Arithmetic functions (Mode 1)	Logic Functions (Mode 0)
0 Addition	0 XOR
1 Substraction	1 AND
2 Increment	2 OR
3 Decrement	3 XNOR
	4 NAND
	5 NOR
	A INV IN1
	B INV IN2
	C IN2
	D IN1
	E LOW
	F HIGH

AU TEST

 


LU TEST

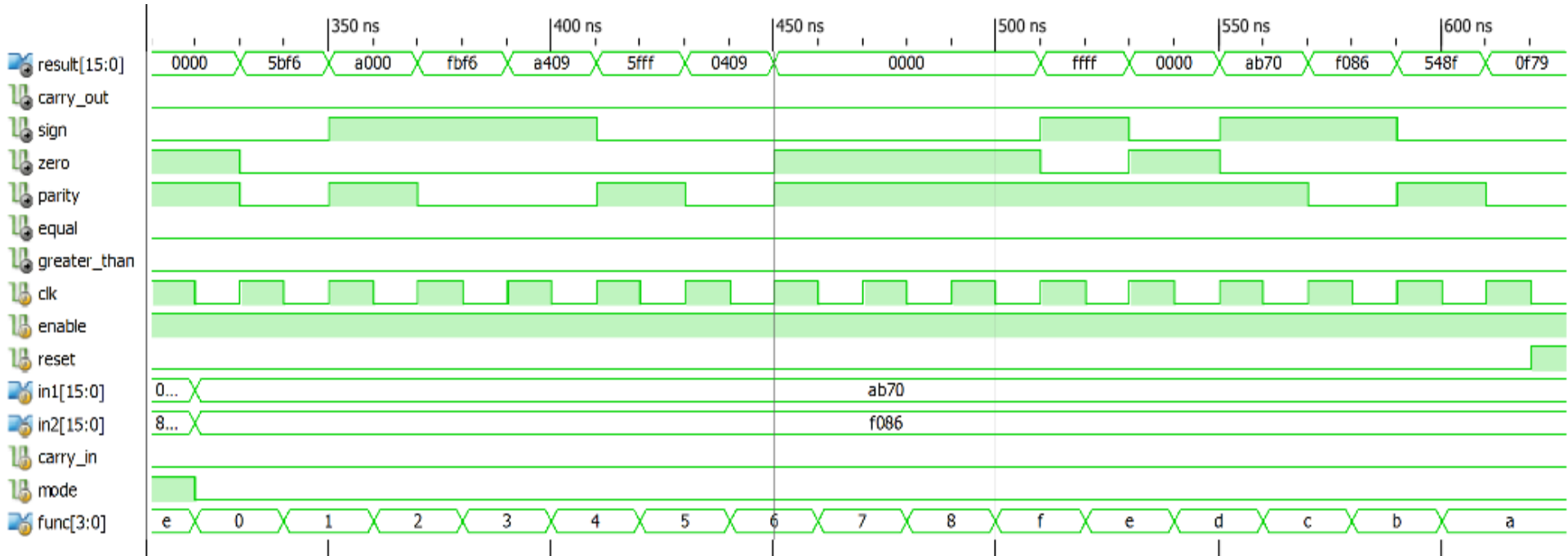

MEMORY



- Two-dimension array of reg variable
- Read, Write and Idle modes
- "\$readmemb" file io system task
- Control output using Enable pin
- Data I/O using same bus
- Memory containing instruction or machine code

TEST MEMORY

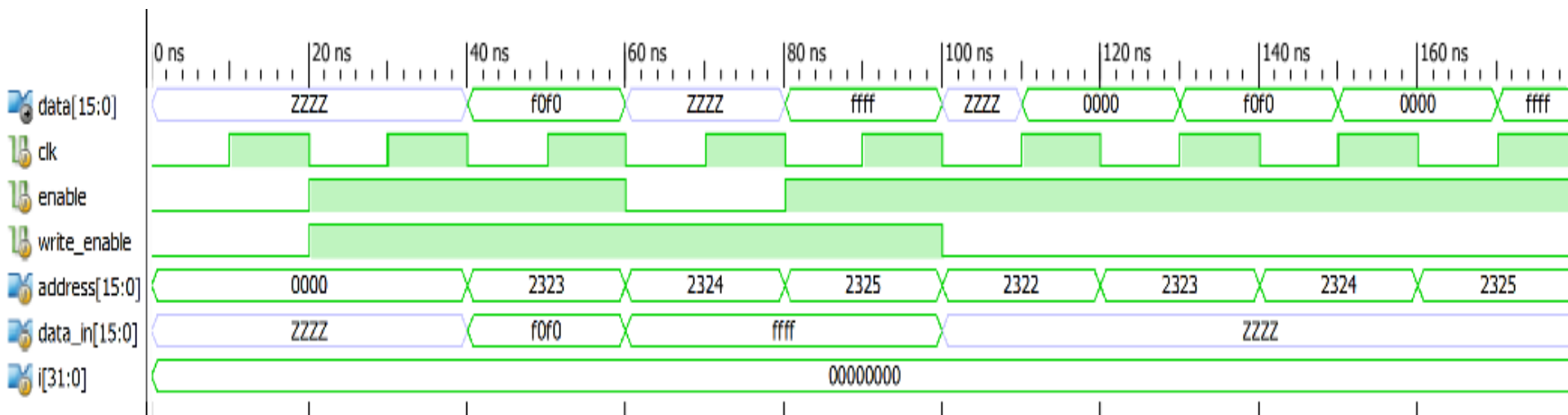


REGISTER

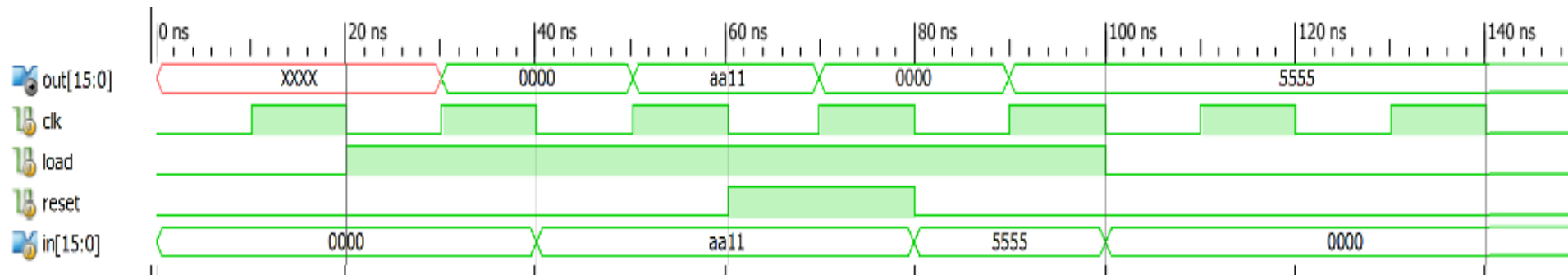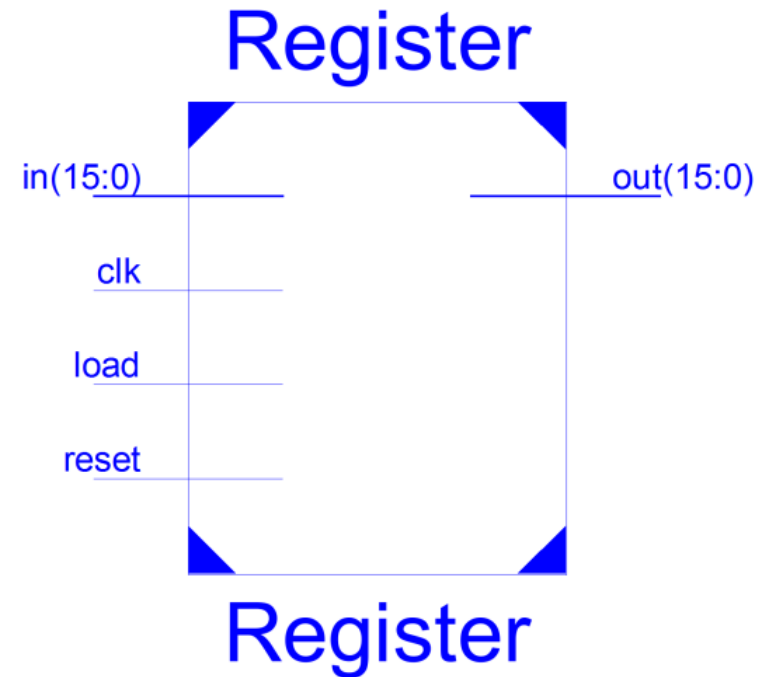- Positive edge triggered
- Control using Load




INSTRUCTION REGISTER

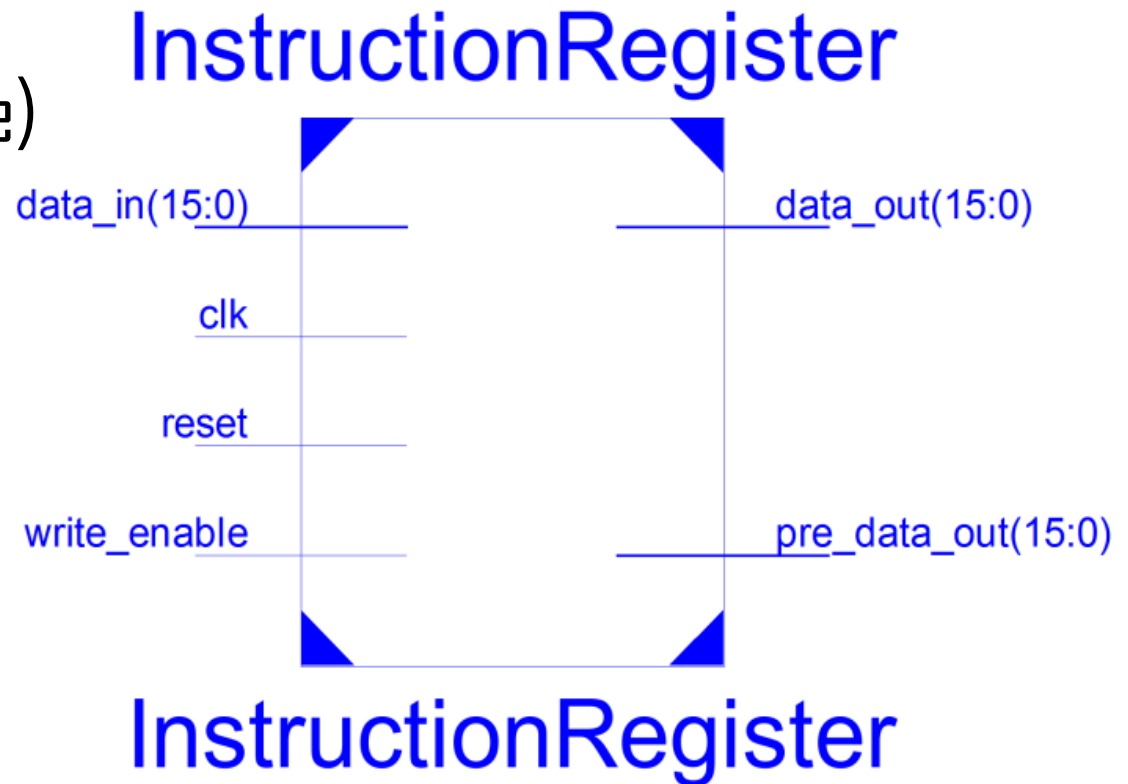- 16-bit
- 4 stage PFU (queue)
- Control using
Write Enable




IR TEST

 

PROGRAM COUNTER


ProgramCounter

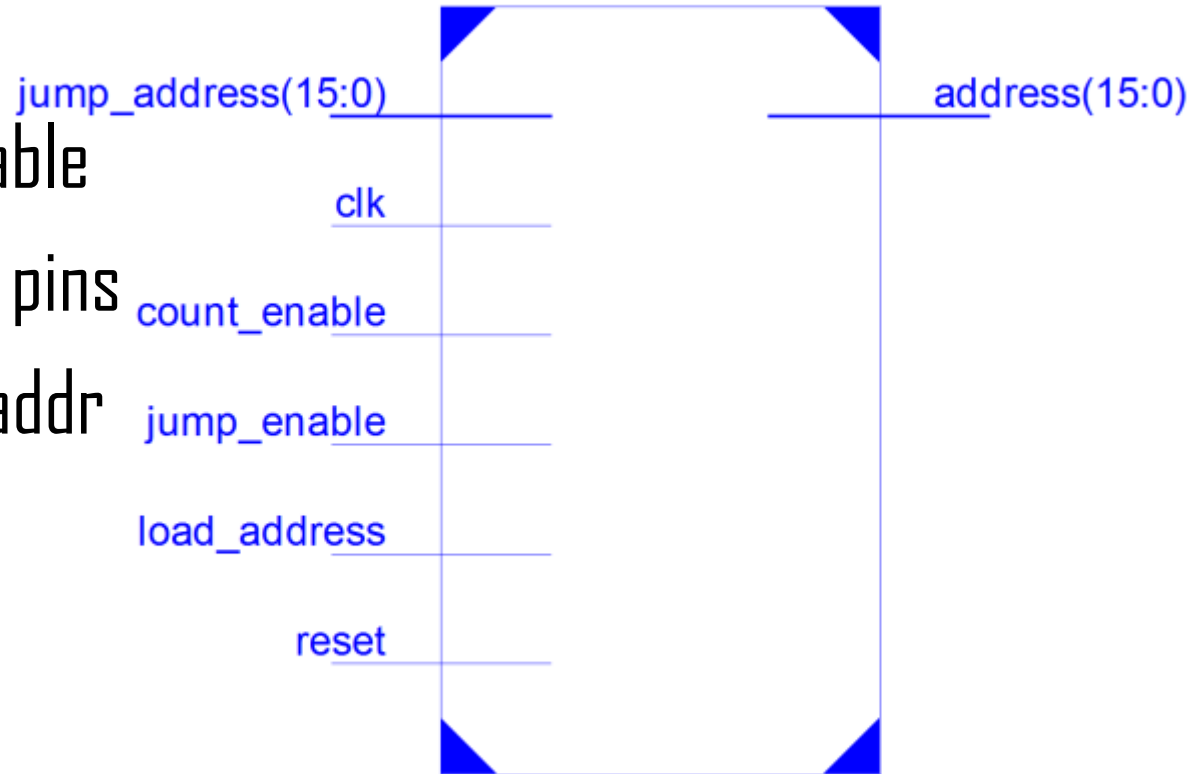- 16-bit counter
- Jump and jump_enable
- Clear, count enable pins
- Control using load addr




ProgramCounter

PC TEST

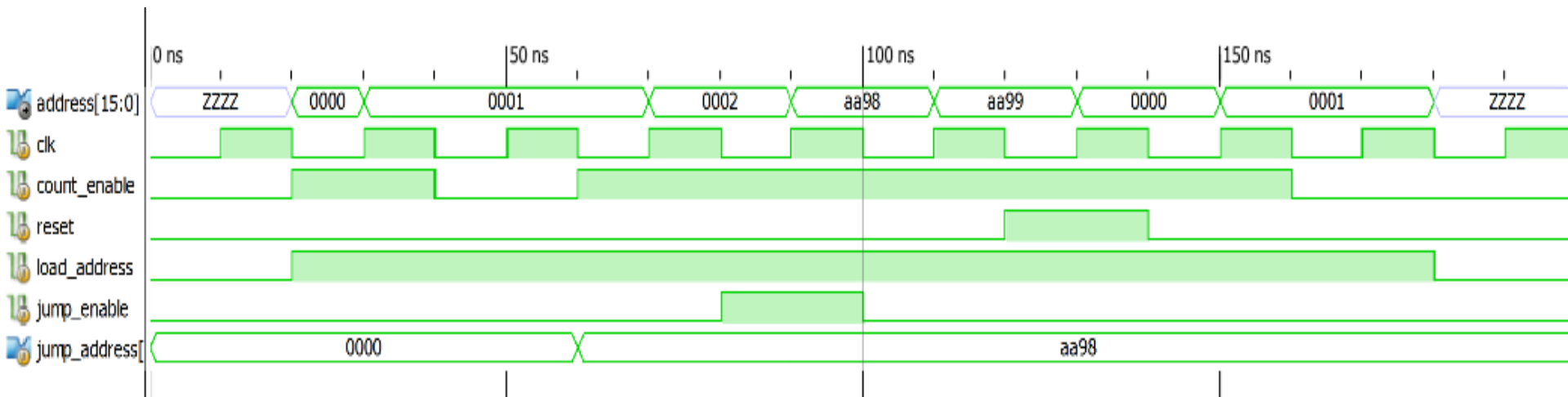


GENERAL PURPOSE REGISTER

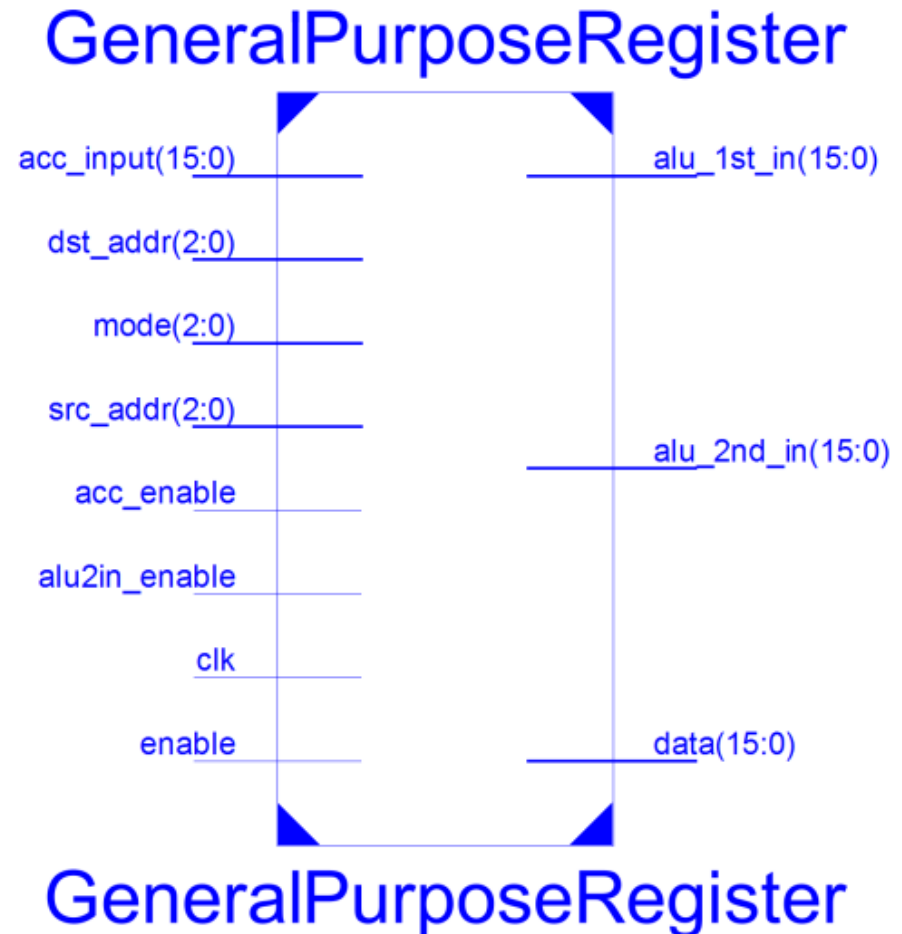- Read, Write, Reg Transfer, Idle modes
- 16-bit registers
- I/O using same data bus
- Src and Dst Addr bus




GPR TEST

 

FLAG REGISTER

- Controlled by ALU
- Useable by Decoder
- 6 – bit


FLAG	Purpose
0	Carry
1	Zero
2	Sign
3	Greater than
4	Equal
5	Parity

 

DECODER/ CONTROL UNIT

- Decodes instruction set
- Generates appropriate control signals
- Commands all components
- Significant component

DECODER BLOCK

 

TOP MODULE


- All components are assembled
- Only clock is provided
- Interconnection of buses and wires

TEST 1

Program :-

NOP	0000
REG R0 // loads data in register 0 to data bus	00ff
REG R1 // loads data in register 1 to data bus	0000
REG R2 // loads data in register 2 to data bus	01ff
LDV R0, 5555H // loads 5555 in register 0	0000
STR R0, [2222H] // stores data in register 0 to memory location 2222	02ff
LDM R1, [2222H] // loads data from memory location 2222 to register 1	0000
NOP	0003
LDR R2, R1 // loads data from register 1 to register 2	5555
NOP	0004
REG R0 // loads data in register 0 to data bus	2222
REG R1 // loads data in register 1 to data bus	0101
REG R3 // loads data in register 1 to data bus	2222
REG R2 // loads data in register 2 to data bus	0000
NOP	0102
	0002
	0000
	00ff
	0000
	01ff
	0000
	03ff
	0000
	02ff
	0000
	0000

SIMULATION

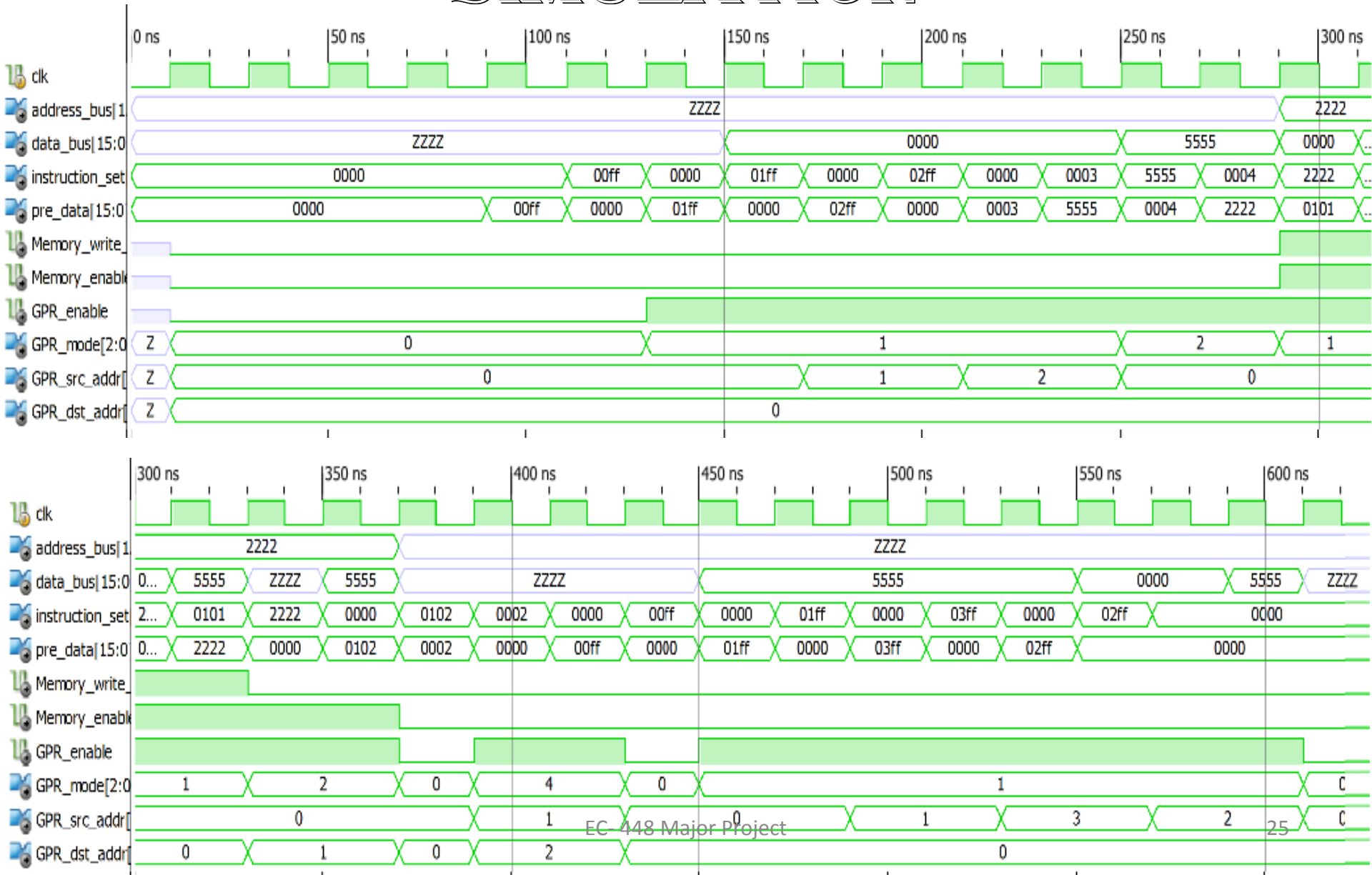


TEST 2


Program :-

	0000
	0003
	8006
NOP	0103
LDV R0, 8006H // loads -6 in register 0 (accumulator)	0006
LDV R1, 0006H // loads 6 in register 1	0010
ADR // adds reg 1 and reg 0 and stores result in accumulator	0000
ADD 0009H // adds 9 to reg 0 and stores in accumulator	0011
SBR // subtracts reg 1 from reg 0	0009
SUB 8004 // subtracts -4 from reg 0	0012
INC // increments value in accumulator	0000
DEC // decrements value in accumulator	0013
REG R0 // loads data in reg 0 (accumulator) to data bus	8004
NOP	0014
	0000
	0015
	0000
	00ff
	0000
	0000

SIMULATION

 

SIMULATION

 


TEST 3


Program :-

	0000
NOP	0003
LDV R0, 3A0FH // loads 3a0f in reg 0 (accumulator)	3A0F
XOR F0F0H // performs xor operation of reg 0 and f0f0	001F
REG R0 // loads data in reg 0 (accumulator) to data bus	F0F0
AND 8888H // performs and operation of reg 0 and 8888	00FF
REG R0 // loads data in reg 0 (accumulator) to data bus	0000
OR 3030H // performs or operation of reg 0 and 3030	001E
REG R0 // loads data in reg 0 (accumulator) to data bus	8888
NOP	00FF
	0000
	001D
	3030
	00FF
	0000
	0000

SIMULATION

 

SIMULATION

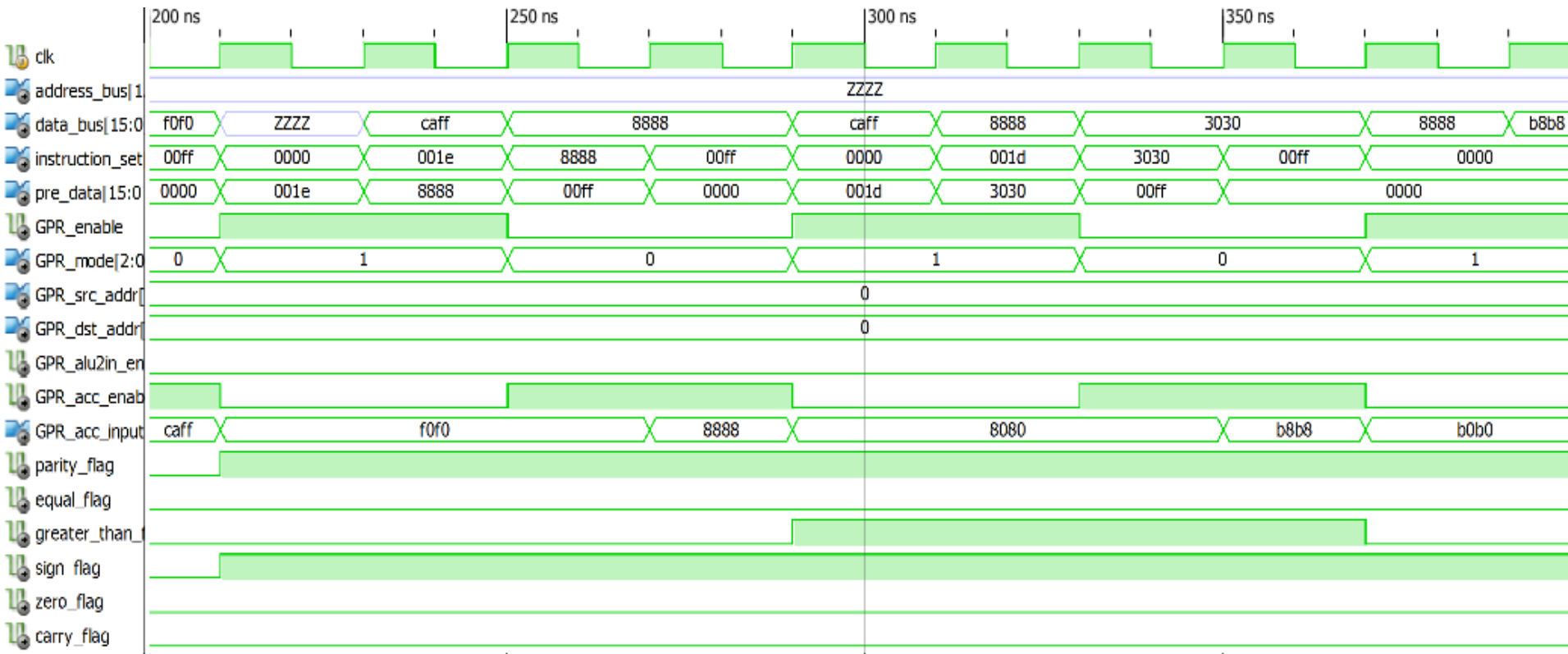


TEST 4


Program :-

	0000
	0003
	ffff
NOP	001e
LDV R0, FFFFH // loads ffff to reg 0	000a
AND 000AH // performs and operation with reg 0 and 00a	0015
DEC // decrease the value of reg 0 by 1	0000
REG R0 // loads data in reg 0 (accumulator) to data bus	00ff
REG R1 // loads data in reg 1 to data bus	0000
LDR R1, R0 // loads data from reg 0 to reg 1	01ff
LDM R0, [1111H] // loads data from memory location 1111 to reg 0	0000
SUB // subtracts reg 1 from reg 0	0002
REG R0 // loads data in reg 0 (accumulator) to data bus	0001
REG R1 // loads data in reg 1 to data bus	0001
NOP	1111
	0012
	0000
	00ff
	0000
	01ff
	0000
	0000

SIMULATION

 

SIMULATION

 

LIMITATIONS

- ALU
- Interrupt handling
- I/O Protocols
- Stack memory and register
- Limited memory interface
- Branch Instructions
- Other

REFERENCES

- NPTEL lecture on microprocessor by Prof. Shantanu
- ARM System Developer's Guide book
- Microprocessors and Interfacing book by Douglass Hall
- GeekforGeeks.org
- Ben eater Youtube Channel
- ChipVerify.com

THANK YOU